

## Circuits

→ Boolean Algebra is used to model the circuitry of electronic devices. Each input and output of such a device can be thought of as a member of the set  $\{0, 1\}$ .  
 $1 \rightarrow \text{ON/HIGH}$   
 $0 \rightarrow \text{OFF/LOW}$


The basic elements of circuits are called logic gates.

→ logic Gates
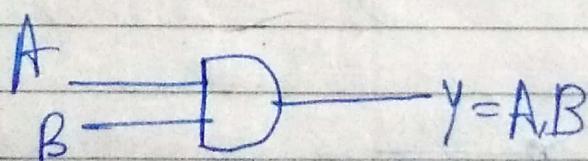
### ① AND Gate


(Boolean Product)

→ It performs 'and' operation it has  $n$  inputs and 1 output




A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

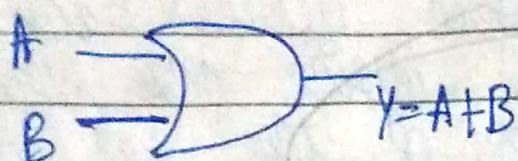② OR GATE (Boolean sum)  
 ↳ It performs OR operation. It has  $n$ -inputs & 1 output




A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

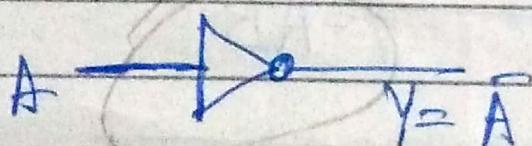③ NOT GATE (Complement)  
 (Inverter) ↳ 1 Input & 1 Output




A	$Y = \bar{A}$
0	1
1	0
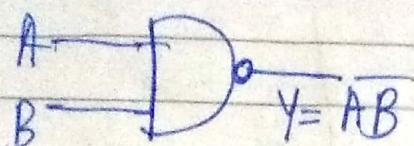
#### ④ NAND GATE (Boolean product complement)




↓

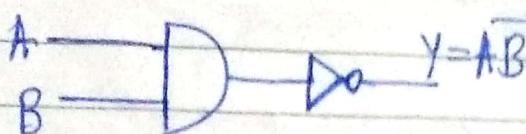


A	B	$Y = \bar{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

#### ⑤ NOR GATE (Boolean sum complement)

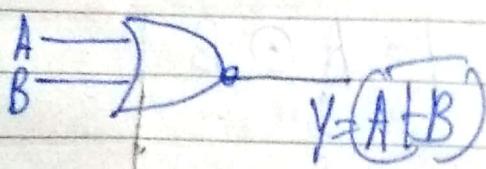

A	B	$Y = \bar{A} + \bar{B}$
0	0	1
0	1	0
1	0	0
1	1	0

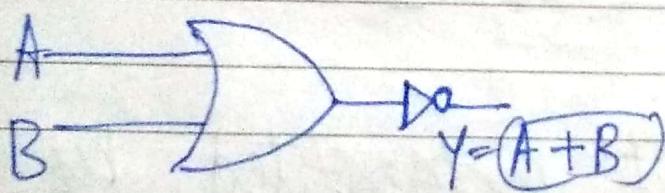

#### ⑥ EX-OR Gate / XOR Gate (Exclusive OR)




$(\text{In sets}) \Rightarrow Y = A \oplus B (\equiv A \cup B - A \cap B = A - B)$

$$A \oplus B = \bar{A}B + A\bar{B} \text{ or } (A \cdot \bar{B})(\bar{A} + B)$$


A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

## ⑦ EX-NOR Gate

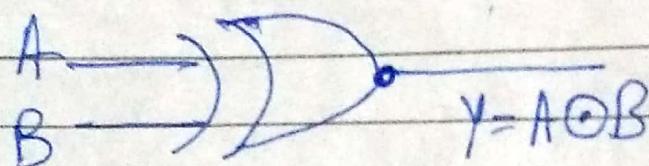


A	B	$Y = A \ominus B$
0	0	1
0	1	0
1	0	0
1	1	1

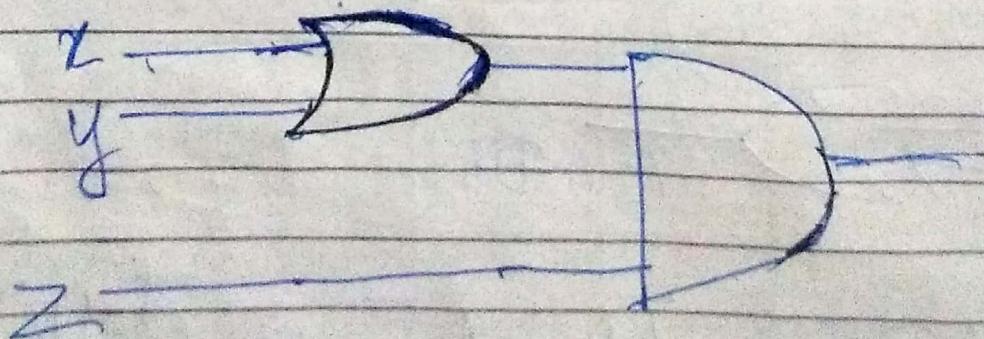Q. Draw the circuit represented by the Boolean function  
 $f(x, y, z) = (x \bar{y})z$




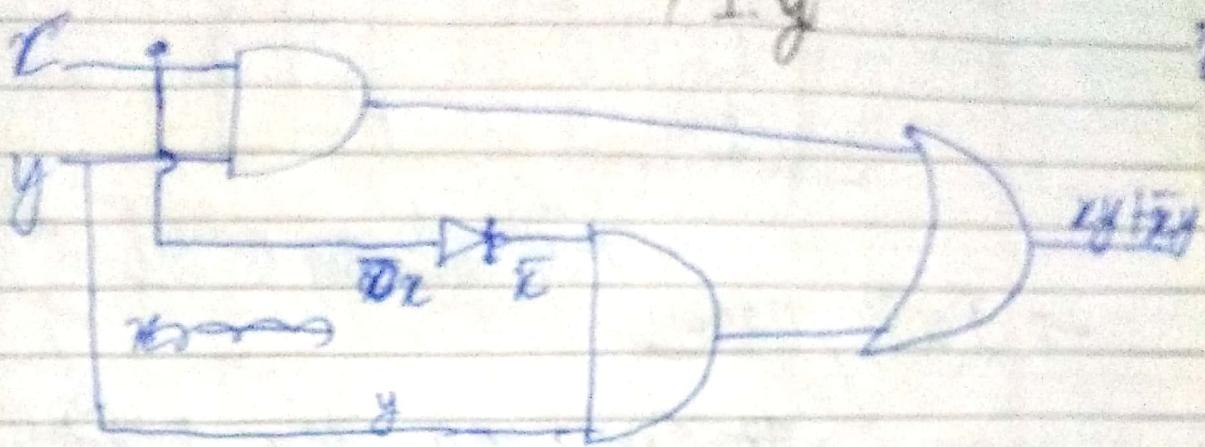
$$Q. f(x,y,z) = xy + \bar{x}y = (\bar{x} + x)y \\ = 1.y$$


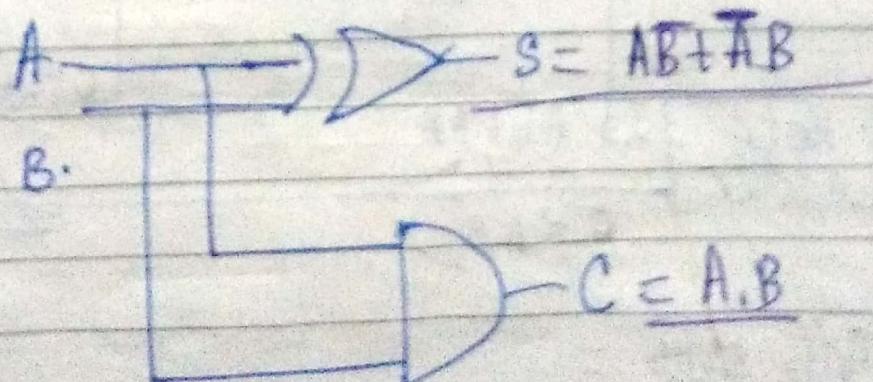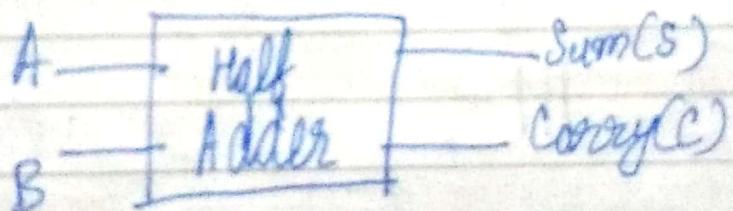
### Half adder



It is a combinational logic circuit with 2 inputs & 2 outputs. It is designed to add 2 single bit binary numbers.



A	B	S	C
0	0	0	0
1	1	1	0
0	1	1	0
1	1	0	1

→ Will add carry as well  
→ Full adder

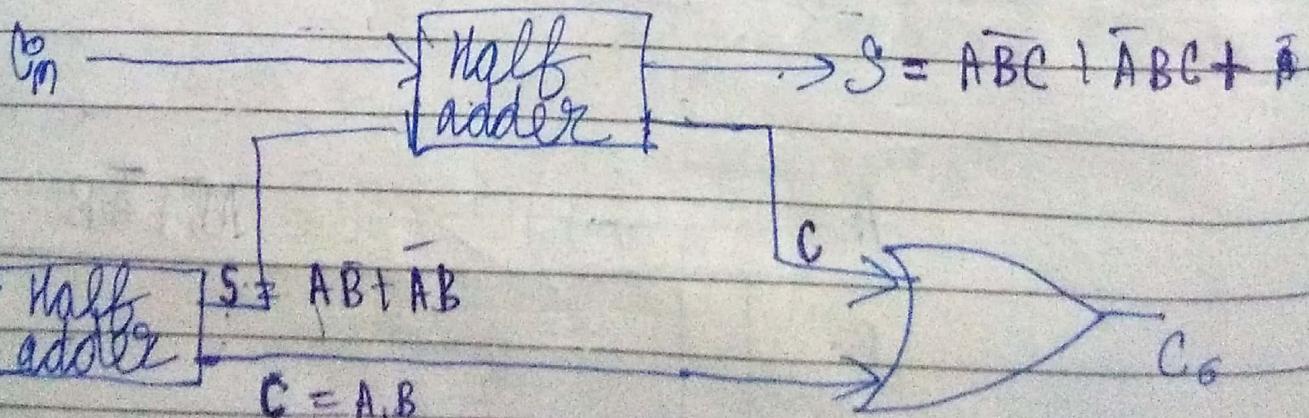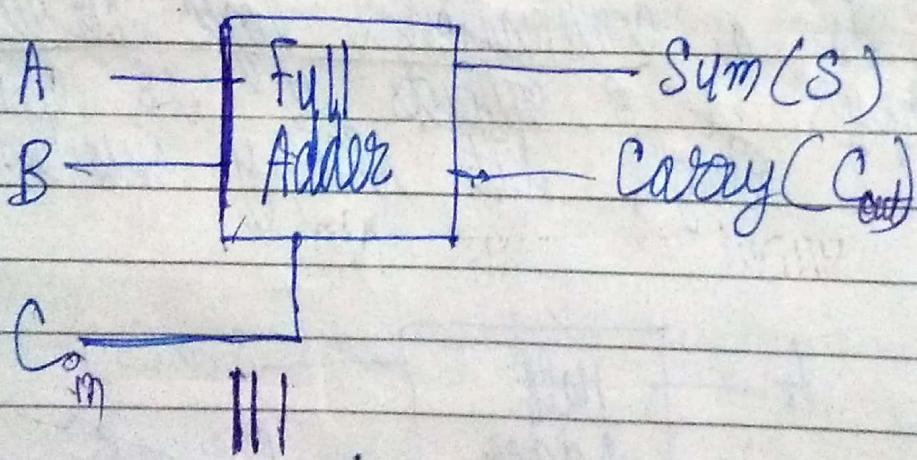→ It can add two 1 bit numbers & carry. Therefore, full adder is 3 input & two outputs device.




A	B	$C_{in}$	$S(A B)$	$C_o$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	1	1
1	1	1	0	1

$$C_o = \overline{A}\overline{B}C_{in} + A\overline{B}C_{in} + A\overline{B}C_{in} + ABC_{in}$$


$$S = \overline{A}\overline{B}C_{in} + \overline{A}BC_{in} + A\overline{B}C_{in} + ABC_{in}$$

Q. Find the output of given CRT.

9)

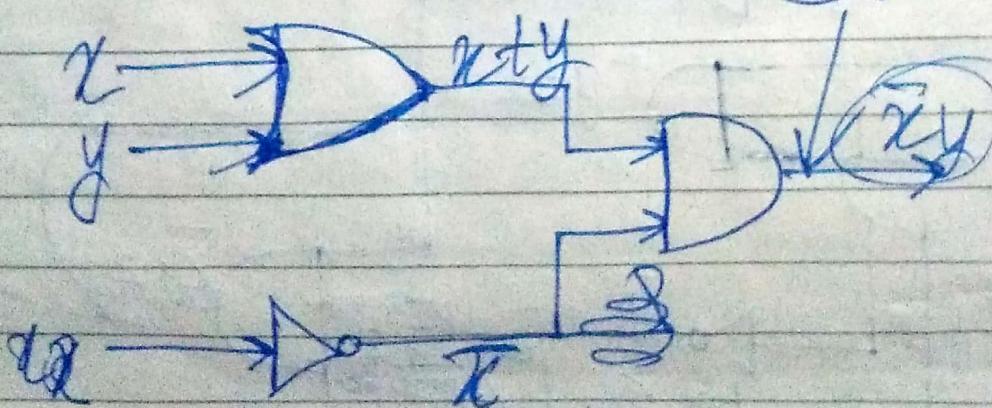

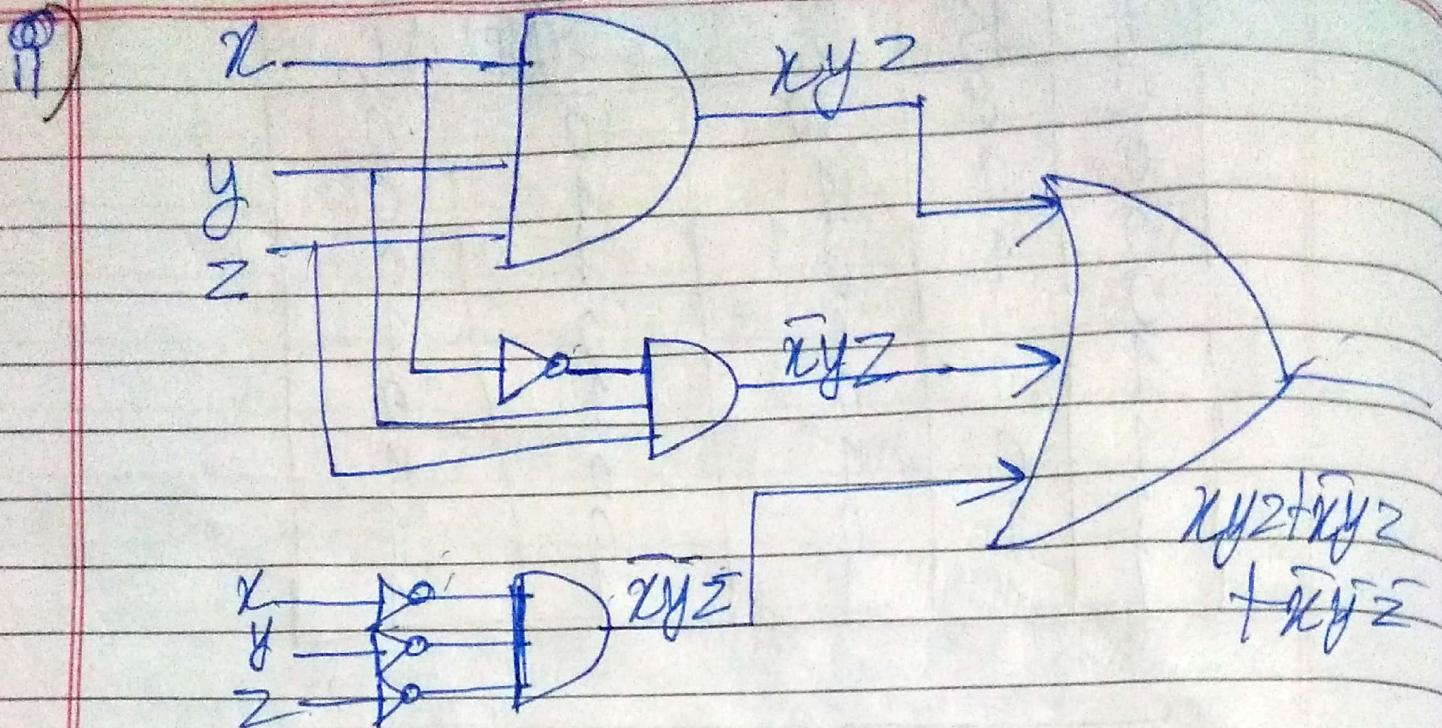
$$(x+y) \cdot \bar{x} = x\bar{x} + y\bar{x} \\ = 0 + \bar{x}y$$



$$XYZ + \bar{X}YZ + \bar{X}\bar{Y}Z = [YZ + \bar{X}YZ]$$

$\hookrightarrow$  Minimized Circuit

→ Minimization of Circuit

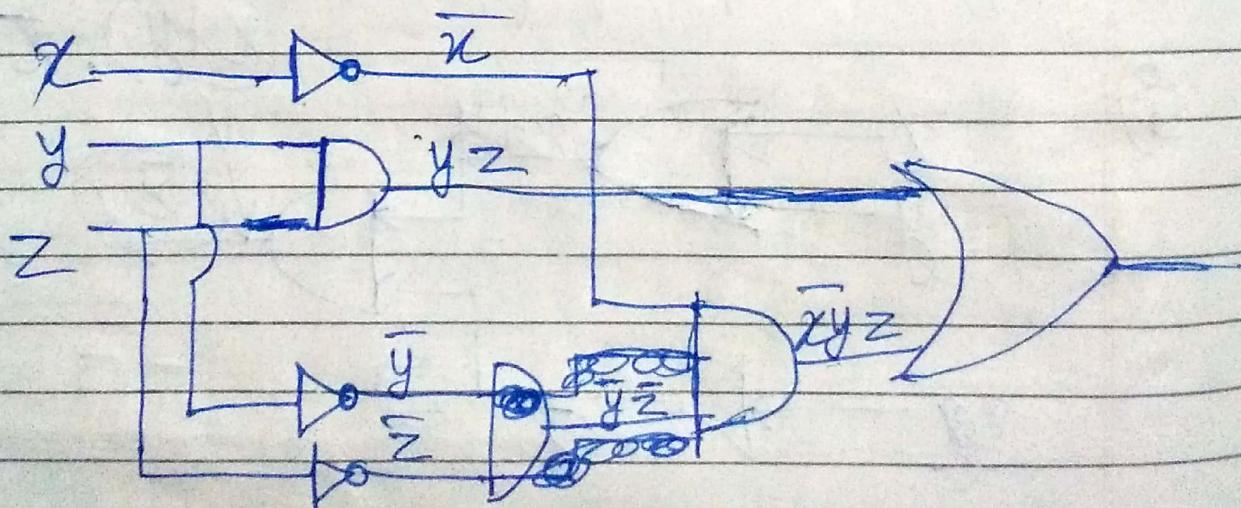

The goal is to produce boolean sums of boolean products that represents a boolean expression with fewest products of literals such that these products

MIRAJ  
Page No. \_\_\_\_\_  
Date. \_\_\_\_\_

contain the fewest literals possible among all S.O.P.s that represent a Boolean function. Finding such a S.O.P. is called minimization of Boolean functions. Minimizing a Boolean function  $\rightarrow$  C.D.N.F)

